

# Proiect CEL Final

**Tema:** ELEMENTE DE PROIECTARE PENTRU  
STABILIZATOARELE DE TENSIUNE CONTINUĂ

**Nume:** Borș Dorin

**Grupa:** 4LF494

**Data:** 01.07.2021

Date de început:

$$U_1 = 8 \quad U_2 = 33$$

$$I_1 = 0,3 \quad I_2 = 4$$

## PROIECT I

### CALCULUL TRANSFORMATORULUI DE REȚEA

1.1.  $P_{u_k} = U_k \cdot I_k$

$$P_{u_1} = 8 \cdot 0,3 = 2,4$$


$$P_{u_2} = 33 \cdot 4 = 132$$

1.2  $P_{tot1} = P_{u_1} + (0,3 \cdot 0,5) P_{tot1}$

Plaja de tens. de ieșire 5...45V

$$A(0,3; 45)$$

$$B(0,5; 5)$$

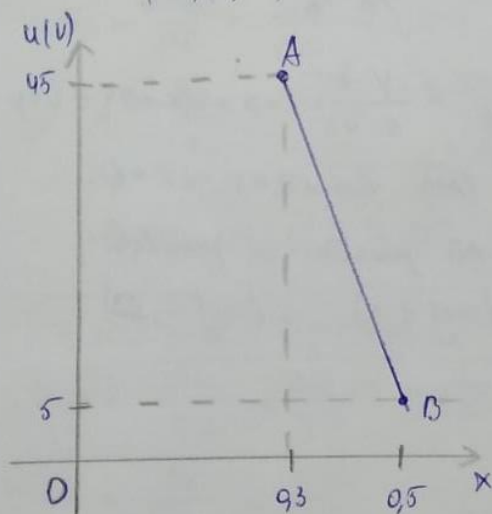

Ec. dreptei AB:

$$\frac{x - x_A}{x_B - x_A} = \frac{y - y_A}{y_B - y_A}$$

$$\frac{x - 0,3}{0,5 - 0,3} = \frac{y - 45}{5 - 45} \Rightarrow$$

$$\Rightarrow -40x + 12 = 0,2y - 3 \Rightarrow$$

$$(AB): 40x + 0,2y - 21 = 0$$

Pe dreapta se află 2 puncte:

$$C(\text{coef } 1; 8) ; D(\text{coef } 2; 33)$$

$$\cdot C(\text{coef } 1, 8) \rightarrow y = 8$$

$$40 \cdot \text{coef } 1 + 0,2 \cdot 8 - 21 = 0 \Rightarrow$$

$$40 \text{ coef } 1 = 19,4$$

$$\text{coef } 1 = 0,485$$

$$\cdot D(\text{coef } 2, 33) \rightarrow y = 33$$

$$40 \cdot \text{coef } 2 + 0,2 \cdot 33 - 21 = 0 \Rightarrow$$

$$40 \text{ coef } 2 = 14,4$$

$$\text{coef } 2 = 0,36$$

$$P_{tot1} = P_{u1} + coef_1 \cdot P_{tot1} \Rightarrow$$

$$P_{u1} + coef_1 \cdot P_{tot1} - P_{tot1} = 0 \Rightarrow$$

$$P_{u1} - P_{tot1}(1 - coef_1) = 0 \Rightarrow$$

$$P_{u1} = P_{tot1}(1 - coef_1) \Rightarrow P_{tot1} = \frac{P_{u1}}{1 - coef_1}$$

$$\left( \cancel{P_{tot1}} = \frac{2,4}{1 - 0,485} \right) P_{tot1} = \frac{2,4}{0,515} = 4,66 \text{ W}$$

$$P_{tot2} = \frac{132}{1 - 0,36} = \frac{132}{0,64} = 206,25 \text{ W}$$

13  $U_{s1} = (1,1 \dots 1,5) U_1$

Fie pntz  $A(1,1; 45)$   
 $B(1,5; 5)$


$$Ec.d2: AB: \frac{x - x_A}{x_B - x_A} = \frac{y - y_A}{y_B - y_A}$$

$$\frac{x - 1,1}{1,5 - 1,1} = \frac{y - 45}{5 - 45} \Rightarrow -40x + 44 = 0,4y - 18$$

$$(AD): 40x + 0,4y - 62 = 0$$

Pe AB plasăm 2 punctele:

$$C(coef_1, 8); D(coef_2, 33);$$

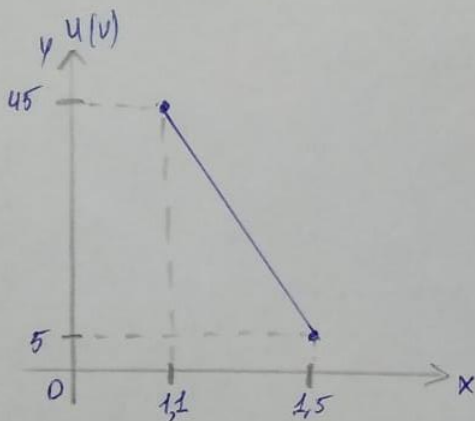

②  $40 coef_1 + 0,4 \cdot 8 - 62 = 0$   
 $coef_1 = 1,47$

①  $40 coef_2 + 0,4 \cdot 33 - 62 = 0$   
 $coef_2 = 1,22$

$$U_{s1} = U_1 \cdot coef_1 = 8 \cdot 1,47 \Rightarrow U_{s1} = 11,76 \text{ V}$$

$$U_{s2} = U_2 \cdot coef_2 = 33 \cdot 1,22 \Rightarrow U_{s2} = 40,26 \text{ V}$$

1.4

$$P = \frac{P_{tot1} + P_{tot2}}{0,9}$$

$$P = \frac{4,66 + 206,25}{0,9} = 234,34 \text{ W}$$

Date de l'input:

$$U_{S1} = 11,76 \text{ V}$$

$$U_{S2} = 40,26 \text{ V}$$

$$P = 234,34 \text{ W}$$

1.5

$$S_m = 30 \text{ cm}^2$$

$$N_0 = 1,6 \text{ spire/V}$$

$$N_{0II} = 1,8 \text{ spire/V}$$

$$y = 2,5 \frac{\text{A}}{\text{mm}^2}$$

$$1.6 \quad n = N_0 \cdot 230 = 1,6 \cdot 230 = 368 \text{ spire}$$

$$n_1 = N_{0II} \cdot U_{S1} = 1,8 \cdot 12 = 21,6 \text{ spire}$$

$$n_2 = N_{0II} \cdot U_{S2} = 1,8 \cdot 40 = 72 \text{ spire}$$

$$1.9 \quad S_0 = \frac{n}{110} = \frac{368}{110} = 3,345$$

$$S_1 = \frac{n_1}{277} = \frac{21,6}{277} = 0,077$$

$$S_2 = \frac{n_2}{18} = \frac{72}{18} = 3,78$$

$$St = S_0 + S_1 + S_2 = 7,202$$

$$1.10 \quad 7,202 < 7,7 \Rightarrow E_{16} \Rightarrow Q = 16$$

$$1.11 \quad C = \frac{S_m}{2Q} = \frac{30}{3,2} = 9,372$$

$$1.12 \quad g_0 = \frac{d_0}{2} = \frac{0,75}{2} = 0,375$$

$$g_1 = \frac{d_1}{2} + d_0 = \frac{0,45}{2} + 0,75 = 0,875$$

$$g_2 = \frac{d_2}{2} + d_1 + d_0 = \frac{1,8}{2} + 0,75 + 0,45 = 2,1$$

$$L_{msp} = 2 \cdot (2e + e) + 2\pi p$$

$$L_{msp0} = 2(2 \cdot 1,6 + 9,372) + 2 \cdot 3,14 \cdot 0,375 = 27,499 \text{ cm}$$

$$L_{msp1} = 2(3,2 + 9,372) + 2 \cdot 3,14 \cdot 0,875 = 31,267 \text{ cm}$$

$$L_{msp2} = 2(3,2 + 9,372) + 2 \cdot 3,14 \cdot 2,1 = 38,332 \text{ cm}$$

$$1.7 \quad I_p = \frac{P}{220} = \frac{234,34 \text{ W}}{220} = 1,065 \text{ A}$$

$$I_{S1} = \frac{P_{tot1}}{U_{S1}} = \frac{4,66 \text{ W}}{11,76 \text{ V}} = 0,396 \text{ A}$$

$$I_{S2} = \frac{P_{tot2}}{U_{S2}} = \frac{206,25 \text{ W}}{40,26 \text{ V}} = 5,12 \text{ A}$$

1.8

$$d_0 = 0,75 \text{ mm}$$

$$d_1 = 0,45 \text{ mm}$$

$$d_2 = 1,8 \text{ mm}$$

1.13

$$L = n \cdot L_{msp}$$

$$L_0 = 368 \cdot 27,5 = 101,2 \text{ m}$$

$$L_1 = 21,6 \cdot 31,267 = 6,753 \text{ m}$$

$$L_2 = 72 \cdot 38,332 = 27,6 \text{ m}$$

1.14

$$R = L \cdot p_1$$

$$R_0 = 101,2 \cdot 0,0384 = 3,887$$

$$R_1 = 6,753 \cdot 0,1082 = 0,737$$

$$R_2 = 27,6 \cdot 0,00684 = 0,188$$

$$1.15 \quad R_{t21} = R_1 + \left(\frac{n_1}{n}\right)^2 \cdot R_0 = 0,737 + \left(\frac{21,6}{368}\right)^2 \cdot 3,887 = 0,75 \Omega$$

$$R_{t22} = R_2 + \left(\frac{n_2}{n}\right)^2 \cdot R_0 = 0,188 + \left(\frac{72}{368}\right)^2 \cdot 3,887 = 0,338 \Omega$$



$$U_1 = 8$$

$$U_2 = 33$$

$$U_{S1} = 12 \text{ V}$$

$$U_{S2} = 40 \text{ V}$$

Date de  
input:

$$I_1 = 0,3$$

$$I_2 = 4$$

$$R_{t21} = 0,75 \Omega$$

$$R_{t22} = 0,338 \Omega$$

PROIECT II CALCULUL REDRESORULUI SI FILTRULUI C  
2.1 P/u tensiunii mai se alege redresorul punct:

$U_1 = 8 \text{ V}$  — stabilizator monoalternant

$U_2 = 33 \text{ V}$  — stabilizatorul punct

2.2 Fie punct  $A \begin{pmatrix} x_A \\ y_A \end{pmatrix} \begin{pmatrix} 0,02 \\ 0,15 \end{pmatrix}$   
 $B \begin{pmatrix} x_B \\ y_B \end{pmatrix} \begin{pmatrix} 0,2 \\ 5 \end{pmatrix}$

ECUATIA DR:  $\frac{x-x_A}{x_B-x_A} = \frac{y-y_A}{y_B-y_A}$

$$\frac{x-0,02}{0,2-0,02} = \frac{y-0,15}{5-0,15} \Rightarrow (x-0,02) 4,85 = (y-0,15) 0,18 \Rightarrow$$

$$\Rightarrow 4,85x - 0,037 = 0,18y - 0,027 \Rightarrow$$

$$\Rightarrow 4,85x - 0,18y - 0,037 + 0,027 = 0 \Rightarrow$$

$$\Rightarrow 4,85x - 0,18y - 0,07 = 0$$

p/u de AB se aleg punctele:

C ( $I_{st1} ; 0,3$ )

D ( $I_{st2} ; 4$ )

• C ( $y = 0,3$ )

$$4,85x - 0,18 \cdot 0,3 - 0,07 = 0$$

$$4,85x = 0,124$$

$$x = \frac{0,124}{4,85} = 0,025 \text{ A}$$

$$\Rightarrow I_{st1} = 0,025 \text{ A}$$

• D ( $y = 4$ )

$$4,85x - 0,18 \cdot 4 - 0,07 = 0$$

$$4,85x = 0,79$$

$$x = 0,162$$

$$I_{st2} = 0,162 \text{ A}$$

2.3

$$I_{R1} = I_1 + I_{st1} = 0,3 + 0,025 = 0,325 \text{ A}$$

$$I_{R2} = I_2 + I_{st2} = 4 + 0,162 = 4,162 \text{ A}$$

$$I_{S1} = I_{R1} = 0,325 \text{ A} \Rightarrow \text{aleg } 1 \text{ N } 4001$$

$$I_{S2} = I_{R2} = 4,162 \text{ A} \Rightarrow \text{aleg punct } K2402$$

2.4

$$U_{max1} = 2 \cdot 12 \text{ V} = 24 \text{ V}$$

$$U_{max2} = 2 \cdot 40 \text{ V} = 80 \text{ V}$$

$$U_{d1} = U_{S1} \cdot \sqrt{2} = 12 \cdot 1,414 = 16,868 \approx 17 \text{ V}$$

$$U_{d2} = U_{S2} \cdot \sqrt{2} = 40 \cdot 1,414 = 56,56 \approx 56,6 \text{ V}$$

$$R_{d1} = \frac{\Delta U}{\Delta I} = 0,2 \Omega$$

$$R_{d2} = \frac{\Delta U}{\Delta I} = 0,025 \Omega$$

2.5

$$U_{e1m} = U_1 + U_{st1m} = U_1 + (5 \dots 10) \text{ V}$$

$$A(5;5)$$

$$B(10;45)$$

$$\frac{x-x_A}{x_B-x_A} = \frac{y-y_A}{y_B-y_A} \Rightarrow \frac{x-5}{10-5} = \frac{y-5}{45-5} \Rightarrow$$

$$40(x-5) = 5(y-5) \Rightarrow 40x - 5y - 175 = 0$$

$$C(U_{s1m}; 12)$$

$$D(U_{s2m}; 40)$$

$$40x - 5y - 175 = 0$$

$$\bullet C(y = 12)$$

$$40x - 5 \cdot 12 = 175 = 0$$

$$x = \frac{235}{40} = 5,875 \Rightarrow U_{s1m} = 5,875 \text{ V}$$

$$\bullet D(y = 40)$$

$$U_{e1m} = 12 + 5,875 = 17,875 \text{ V}$$

$$40x - 5 \cdot 40 - 175 = 0$$

$$x = \frac{375}{40} = 9,375 \text{ V} \Rightarrow U_{s2m} = 9,375 \text{ V}$$

2.6

$$U_{s1M} = 17 \text{ V}$$

$$U_{s2M} = 56,6 \text{ V}$$

$$U_{e2m} = 40 + 9,375 \text{ V} = 49,375 \text{ V}$$

$$U_{R1} = I_{R1} \cdot R_{R1} = 0,325 \text{ A} \cdot R_{R1}$$

$$U_{R1} = \frac{U_{e1M} + U_{e1m}}{2}$$

$$\Rightarrow R_{R1} = \frac{U_{e1M} + 17,875 \text{ V}}{0,65}$$

$$\Rightarrow 0,325 \cdot R_{R1} = \frac{U_{e1M} + U_{e1m}}{2} \Rightarrow$$

$$U_{e1M} = \frac{(U_{s1M} - U_0) R_{R1}}{R_{R1} + R_{t21} + R_{d1}} = \frac{(17 - 0,7) \cdot R_{R1}}{R_{R1} + 0,75 + 0,2} = \frac{16,3 \cdot R_{R1}}{0,95 + R_{R1}} = \frac{16,3 \cdot \frac{U_{e1M} + 17,875}{0,65}}{0,95 + \frac{U_{e1M} + 17,875}{0,65}}$$

$$= \frac{25,076(U_{e1M} + 17,875)}{\frac{U_{e1M} + 17,875 + 0,6175}{0,65}} = \frac{16,3(U_{e1M} + 17,875)}{U_{e1M} + 18,5} = \frac{16,3 U_{e1M} + 291,36}{U_{e1M} + 18,5}$$

$$U_{e1M}(U_{e1M} + 18,5) = 16,3 U_{e1M} + 291,36$$

$$U_{e1M}^2 + U_{e1M} 18,5 - 16,3 U_{e1M} - 291,36 = 0$$

$$U_{e1M}^2 + 2,2 U_{e1M} - 291,36 = 0$$

$$\Delta = 4,84 - 4 \cdot (-291,36) \cdot 1 = 4,84 + 1165,44 = 1170,28$$

$$U_{e1M1} = \frac{-2,2 - \sqrt{1170,28}}{2} < 0$$

$$U_{e1M2} = \frac{-2,2 + \sqrt{1170,28}}{2} = \frac{-2,2 + 34,2}{2} = \frac{32}{2} = 16 \text{ V}$$

$$U_{R1} = \frac{U_{C1M} + 17,875}{2} = \frac{16 + 17,875}{2} = 16,93 \text{ V}$$

$$R_{R1} = \frac{U_{R1}}{I_{R1}} \Rightarrow \frac{16,93 \text{ V}}{0,325 \text{ A}} = 52,092 \Omega$$

$$U_{R2} = I_{R2} \cdot R_{R2} = 4,162 \text{ A} \cdot R_{R2}$$

$$U_{R2} = \frac{U_{C2M} + U_{C2m}}{2} \Rightarrow$$

$$4,162 \cdot R_{R2} = \frac{U_{C2M} + U_{C2m}}{2}$$

$$R_{R2} = \frac{U_{C2M} + 48,375}{8,324}$$

$$U_{C2M} = \frac{(U_{S2M} - U_0) \cdot R_{R2}}{R_{t22} + R_{d2} + R_{R2}} = \frac{(56,6 - 1,4) \cdot R_{R2}}{0,338 + 0,025 + R_{R2}} = \frac{55,2 \cdot R_{R2}}{0,364 + R_{R2}}$$

$$= \frac{55,2 \cdot \left( \frac{U_{C2M} + 48,375}{8,324} \right)}{0,364 + \left( \frac{U_{C2M} + 48,375}{8,324} \right)} = \frac{55,2 (U_{C2M} + 48,375)}{U_{C2M} + 52,404}$$

$$U_{C2M} (U_{C2M} + 52,404) = 55,2 U_{C2M} + 2725,5$$

$$U_{C2M}^2 + 52,404 U_{C2M} - 55,2 U_{C2M} - 2725,5 = 0$$

$$U_{C2M}^2 - 2,8 U_{C2M} - 2725,5 = 0$$

$$\Delta = 7,84 + 10802 = 10809,84$$

$$U_{C2M1} = \frac{-b - \sqrt{\Delta}}{2a} = \frac{2,8 - \sqrt{\Delta}}{2} < 0$$

$$U_{C2M2} = \frac{2,8 + \sqrt{10809,84}}{2 \cdot 1} = \frac{2,8 + 104,45}{2} = 53,625 \text{ V}$$

$$U_{C2M} = 53,625 \text{ V}$$

$$U_{R2} = \frac{53,625 + 48,375}{2} = 51,5 \text{ V}$$

$$R_{R2} = \frac{U_{R2}}{I_{R2}} = \frac{51,5 \text{ V}}{4,162 \text{ A}} = 12,373 \Omega$$

$$27 \Delta U_{Ci} = (U_{Cin} - U_{Cim}) = \frac{U_{Cim} T}{R_{Ri} C_i}$$

$$C_2 = \frac{1,0725}{4,25 \cdot 12,373} = 20312 \text{ pF}$$

$$\Delta U_{C1} = (16 - 17,875) = \frac{16 \cdot 902}{52,092 C_1} \Rightarrow$$

$$-82,67 C_1$$

$$-1,875 = 0,32$$

$$C_1 = 3276 \text{ pF}$$

⑥



$$U_1 = 8 \quad U_{C1m} = 17,875 \text{ V}$$

$$I_1 = 0,3 \quad U_{S1} = 12 \text{ V}$$

Date de început:

## PROIECT III

### CALCULUL

### STABILIZATORULUI

$$I_{B1} = \frac{I_1}{\beta_m}$$

$$\beta_m = 40$$

$$I_{B1} = \frac{0,3}{40} = 0,0075 \text{ A}$$

$$I_{B1} = 7,5 \text{ mA}$$

3.1

$$I_{em} > I_1 = 0,3 \text{ A}$$

$$U_{CBO} > U_{S1H} = 17 \text{ V}$$

$$T \Rightarrow [BD 137]$$

$$I_c = 1,5 \text{ A}$$

$$V_{CBO} = 60 \text{ V}$$

3.2

$$U_2 = U_1 + 0,7 \text{ V} = 8,7 \text{ V} \quad (\text{tensiunea diodei Zener})$$

3.4

$$P_{D1H} = 1,5 \cdot U_2 \cdot I_{B1}$$

$$P_{D1H} = 1,5 \cdot 8,7 \cdot (0,0075 + 0,5 \cdot 0,0075) = 0,15 \text{ W} \quad (\text{puterea disipată numai pe dioda Zener})$$

3.5 Se alege dioda Zener:

$$\left\{ \begin{array}{l} U = U_Z = 8,7 \text{ V} \\ P_D > P_{D1H} = 0,15 \text{ W} \end{array} \right\} \Rightarrow \text{SMZ 4742}$$

(700 mW)

Determinare valorii R:

$$U_{R1} = U_{C1m} - U_Z > R(I_{B1} + I_{Zm})$$

$$I_{Zm} = 1 \text{ mA}$$

$$17,875 - 8,7 > R(7,5 + 1)$$

$$9,175 > R \cdot 8,5$$

$$R < \frac{9,175}{8,5} = 1,078 \text{ k} = 1078 \Omega$$

$$3.6 \quad U_Z(U_{S1H} - U_Z) / R < P_D$$

$$\frac{8,7(17 - 8,7)}{1078} < P_D$$

$$10^3 \cdot 0,0668 < 700$$

$$66,8 < 700 \quad \checkmark$$

$$U_2 = 33 \quad U_{C2m} = 49,375 \text{ V}$$

$$I_2 = 4 \quad U_{S2} = 40$$

Alegerea tranzistorului T3

$$I_{B1} > 1,05 \cdot I_2 = 4,2 \text{ A}$$

$$U_{CBO} > U_{S2H} = 56,6 \text{ V} \Rightarrow$$

$$\Rightarrow \boxed{\text{TIP 121}} \quad \text{trans. Darlington}$$

$$4.2 \quad U_{C2m} = U_{R2m} + U_{BE3H} + U_2$$

$$I_{BE3H} = \frac{I_{T3H}}{\beta_{3m}} = 0,0042$$

$$\beta_{3m} = 1000$$

$$49,375 = U_{R2m} + 0,7 + 33$$

$$U_{R2m} = 49,375 - 33,7 = 15,675 \text{ V}$$

$$4.3 \quad R_2 < U_{R2m} / I_{B3H}$$

$$R_2 < \frac{15,675}{0,0042} = 3732,14$$

$$R_2 = 2000 \Omega$$



46

Calculul amplificatorului de eroare

$$I_{R2M} = (U_{S2M} - U_2) / R_2 = \frac{56,6 - 33}{2000} = 0,0118 \text{ A (curentul maxim prin tranzistorul } T_2)$$

4.7 Se deg  $T_1$  și  $T_2$  identice:

$$\begin{cases} I_{CM} > I_{R2M} = 11,8 \text{ mA} \\ U_{CEQ} > U_{S2M} = 56,6 \text{ V} \end{cases} \rightarrow \boxed{\text{PZT 3804}}$$

4.8  $I_3 = I_{R2M} = 11,8 \text{ mA}$

$$U_{CE2M} = 3 \text{ V} \Rightarrow U_{R3} = 9,7 + U_2 - 3 \text{ V} = 33 - 2,3 = 30,7 \text{ V} \Rightarrow$$

$$\Rightarrow R_3 = \frac{U_{R3}}{I_3} = \frac{30,7 \text{ V}}{0,0118 \text{ A}} = 2601,7 \Omega$$

4.9  $R_1 = R_2 = 2000 \Omega$

Calculul circuitului tensiunii de referință ( $R, D_2$ )

4.10  $U_2 = U_{R3} + 0,7 \text{ V} = 31,4 \text{ V}$  (Tensiunea Zener)

4.11  $\begin{cases} P = 0,5 \text{ W} \\ U_2 = 31,4 \text{ V} \end{cases} \Rightarrow \boxed{1N5256}$

4.12  $I_{7M} \Rightarrow I_3 / \beta_{1M} = \frac{11,8}{60} = 0,196 \text{ mA}$

$$U_{RM} = U_{CE2M} - U_2 = 48,375 - 31,4 = 18 \text{ V}$$

$$R = \frac{U_{RM}}{I_{7M}} = \frac{18}{0,196 \cdot 10^{-3}} = 91,8 \text{ k}\Omega$$

Calculul divizorului rezistor

4.13  $0,05 \cdot I_2 > I_4 \Rightarrow I_{7M} / \beta_{2M}$

$$I_4 < 0,05 \cdot 4 = 0,2 \text{ A}$$

$$I_4 \Rightarrow I_{7M} / \beta_{2M} = \frac{0,4}{60} = 0,0066 \text{ mA}$$


$$I_4 = 66 \text{ mA}$$

4.14  $R_4 + R_5 = \frac{U_2}{I_4}$



$$R_5 = \frac{U_{R5}}{I_4} = \frac{31,4}{66 \text{ mA}} = \frac{31,4}{0,066} = 475 \Omega$$

$$R_4 + 475 = \frac{33}{0,066} \Rightarrow R_4 = 500 - 475 = 25 \Omega$$

# SCHEMA


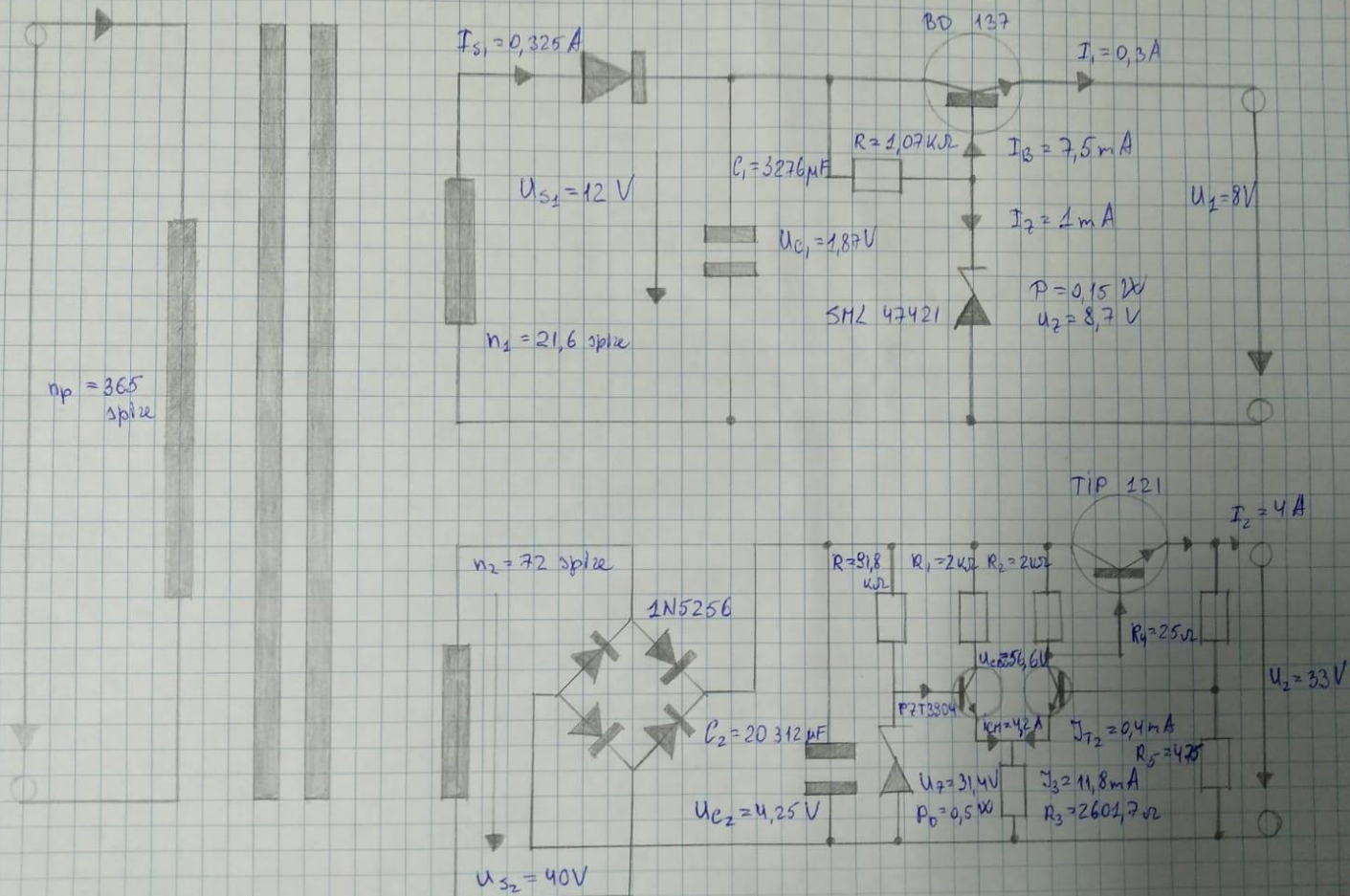


## Schema și simularea 1

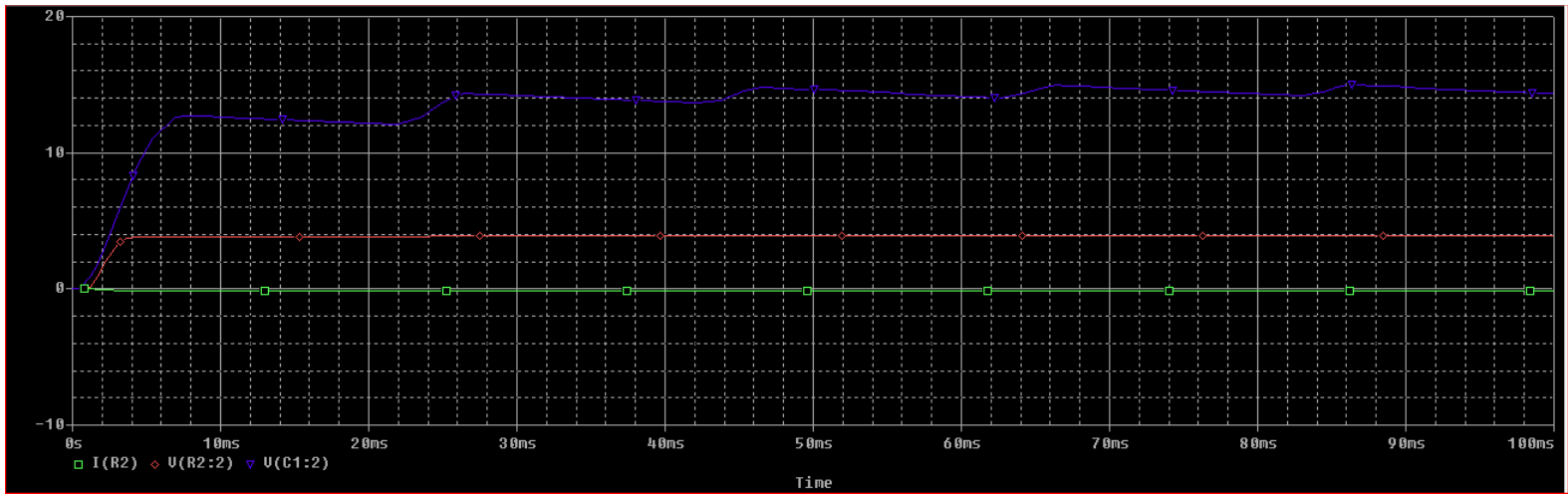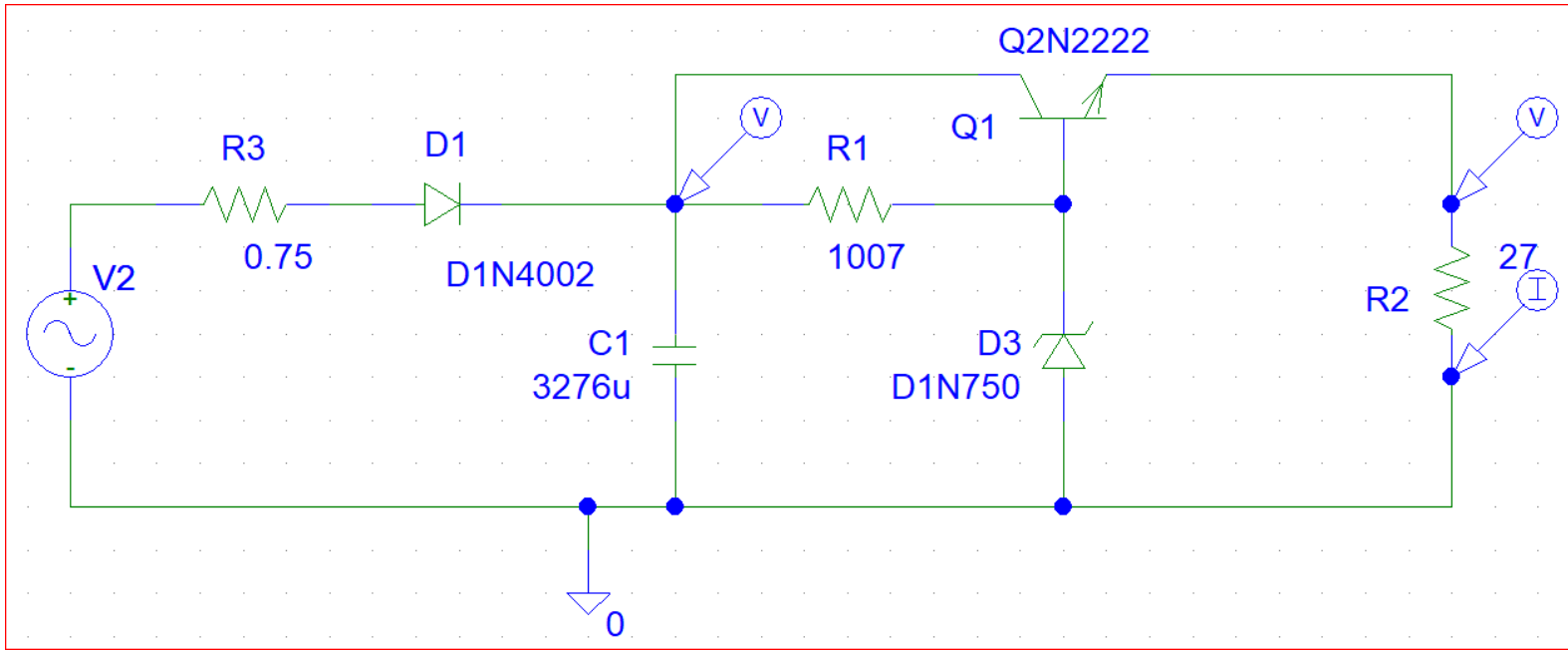



## Schema și simularea 2

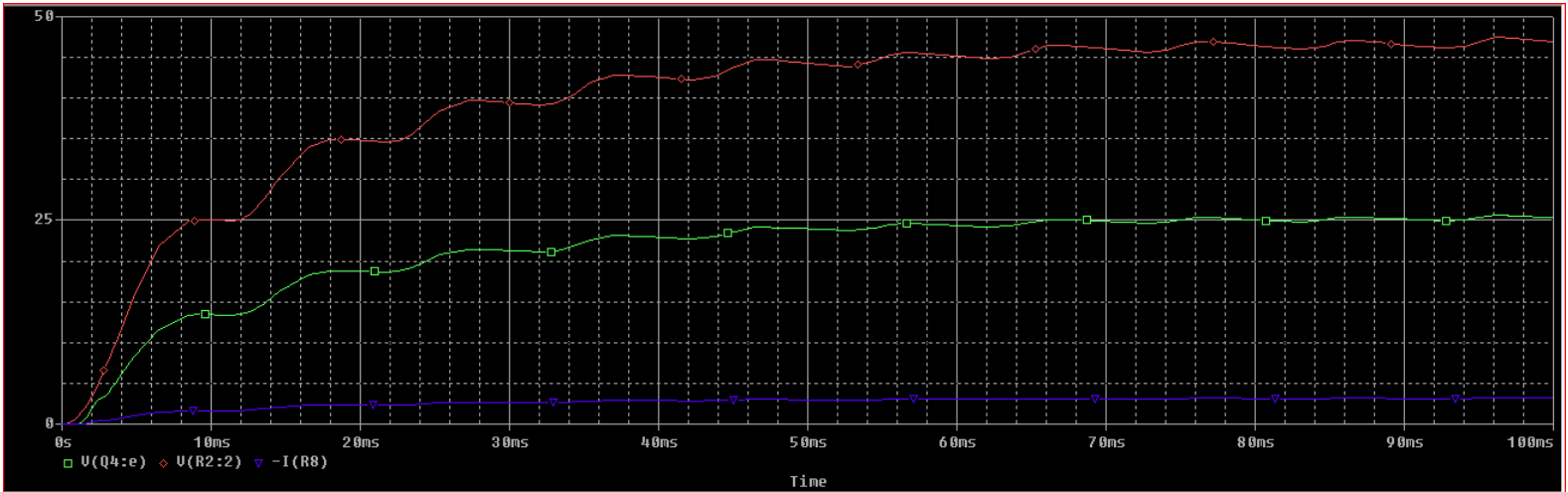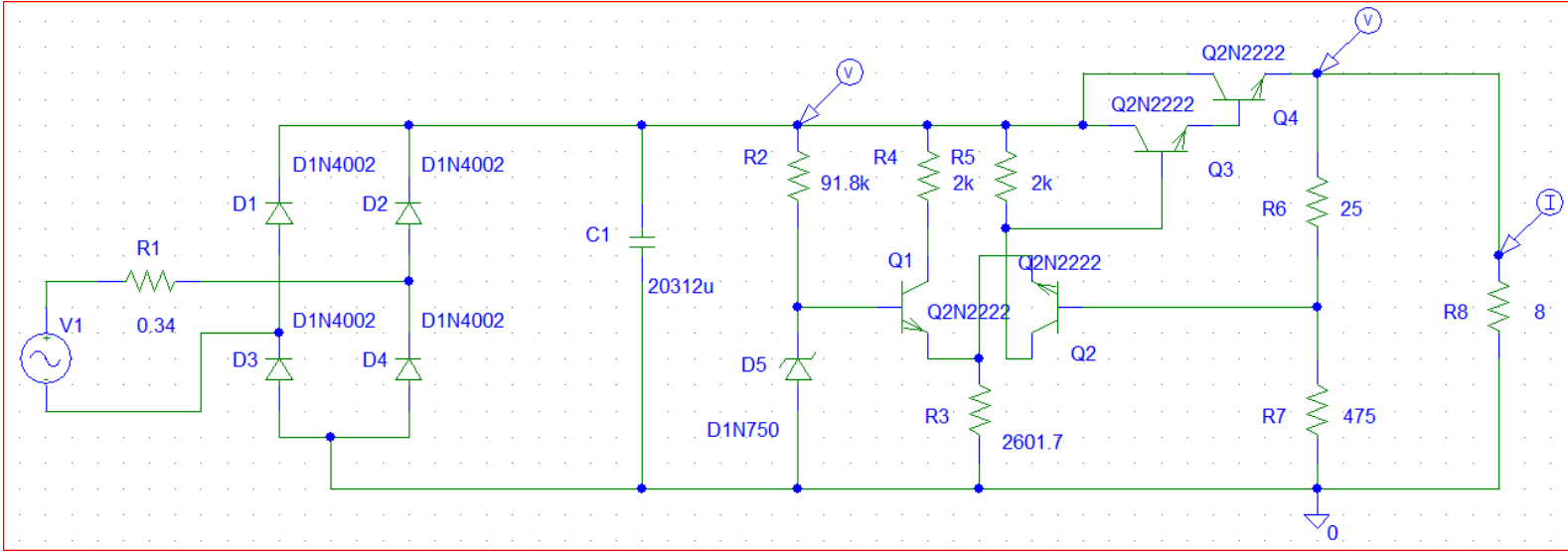

# Foi de catalog



## TIP120/121/122 TIP125/126/127

### COMPLEMENTARY SILICON POWER DARLINGTON TRANSISTORS

- STMicroelectronics PREFERRED  
SALESTYPES


#### DESCRIPTION

The TIP120, TIP121 and TIP122 are silicon Epitaxial-Base NPN power transistors in monolithic Darlington configuration mounted in Jedec TO-220 plastic package. They are intended for use in power linear and switching applications. The complementary PNP types are TIP125, TIP126 and TIP127, respectively.



TO-220

#### INTERNAL SCHEMATIC DIAGRAM

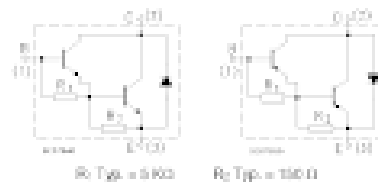

#### ABSOLUTE MAXIMUM RATINGS

Symbol	Parameter	Value				Unit
		NPN	TIP120	TIP121	TIP122	
		PNP	TIP125	TIP126	TIP127	
$V_{CE0}$	Collector-Base Voltage ( $I_C = 0$ )		60	60	60	V
$V_{CE0}$	Collector-Emitter Voltage ( $I_E = 0$ )		60	60	60	V
$V_{BE0}$	Emitter-Base Voltage ( $I_C = 0$ )			5		V
$I_C$	Collector Current			5		A
$I_{CM}$	Collector Peak Current			5		A
$I_B$	Base Current			0.1		A
$P_{tot}$	Total Dissipation at $T_{amb} \leq 25^\circ\text{C}$ $T_{amb} \leq 25^\circ\text{C}$			65		W
				2		W
$T_{stg}$	Storage Temperature			-55 to 150		$^\circ\text{C}$
$T_J$	Max. Operating Junction Temperature			150		$^\circ\text{C}$

\*For PNP types voltage and current values are negative.



Micro Commercial Components  
21201 Itasca Street Chatsworth  
CA 91311  
Phone: (818) 701-4933  
Fax: (818) 701-4938

1N5221  
THRU  
1N5281

## Features


- Wide Voltage Range Available
- Glass Package
- High Temp Soldering: 250°C for 10 Seconds At Terminals

500 mW  
Zener Diode  
2.4 to 200 Volts

## Maximum Ratings


- Operating Temperature: -55°C to +150°C
- Storage Temperature: -55°C to +150°C
- 500 mWatt DC Power Dissipation
- Power Derating: 4.0mW/°C above 50°C
- Forward Voltage @ 200mA: 1.1 Volts

Figure 1 - Typical Capacitance

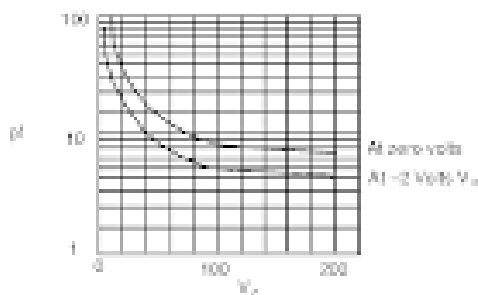


Typical Capacitance (pF) - versus - Zener voltage (V<sub>Z</sub>)

Figure 2 - Derating Curve

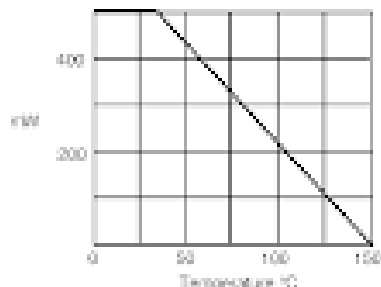

Power Dissipation (mW) - Versus - Temperature °C

DO-35

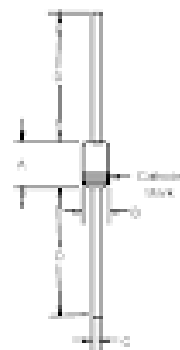

DIM	DIMENSIONS				NOTE
	MIN	MAX	MIN	MAX	
A	---	150	---	4.0	
B	---	325	---	250	
C	---	250	---	25	
D	1.00	---	25.4	---	




# 2N3904 / MMBT3904 / PZT3904

## NPN General Purpose Amplifier
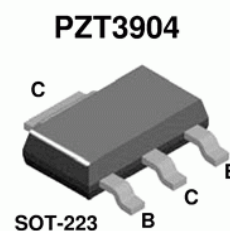
### Features

- This device is designed as a general purpose amplifier and switch.
- The useful dynamic range extends to 100 mA as a switch and to 100 MHz as an amplifier.



### Absolute Maximum Ratings\* $T_a = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Value	Units
$V_{CEO}$	Collector-Emitter Voltage	40	V
$V_{CBO}$	Collector-Base Voltage	60	V
$V_{EBO}$	Emitter-Base Voltage	6.0	V
$I_C$	Collector Current - Continuous	200	mA
$T_J, T_{stg}$	Operating and Storage Junction Temperature Range	-55 to +150	$^\circ\text{C}$

\* These ratings are limiting values above which the serviceability of any semiconductor device may be impaired.

#### NOTES:

- 1) These ratings are based on a maximum junction temperature of 150 degrees C.
- 2) These are steady state limits. The factory should be consulted on applications involving pulsed or low duty cycle operations.

### Thermal Characteristics $T_a = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Max.			Units
		2N3904	*MMBT3904	**PZT3904	
$P_D$	Total Device Dissipation	625	350	1,000	mW
	Derate above $25^\circ\text{C}$	5.0	2.8	8.0	mW/ $^\circ\text{C}$
$R_{\theta JC}$	Thermal Resistance, Junction to Case	83.3			$^\circ\text{C}/\text{W}$
$R_{\theta JA}$	Thermal Resistance, Junction to Ambient	200	357	125	$^\circ\text{C}/\text{W}$

\* Device mounted on FR-4 PCB 1.6" X 1.6" X 0.06".

\*\* Device mounted on FR-4 PCB 36 mm X 18 mm X 1.5 mm; mounting pad for the collector lead min. 6  $\text{cm}^2$ .

SILICON NPN EPITAXIAL TYPE (PCT PROCESS)

**BD135**  
**BD137**  
**BD139**

MEDIUM POWER AMPLIFIER APPLICATIONS.


FEATURES:

- Designed for Complementary Use with BD136, BD138 and BD140.

MAXIMUM RATINGS ( $T_a=25^{\circ}\text{C}$ )

CHARACTERISTIC		SYMBOL	RATING	UNIT
Collector-Base Voltage	BD135	$V_{CB0}$	45	V
	BD137		60	
	BD139		80	
Collector-Emitter Voltage	BD135	$V_{CE0}$	45	V
	BD137		60	
	BD139		80	
Emitter-Base Voltage		$V_{EB0}$	5	V
Collector Current	DC	$I_C$	0.5	A
	Peak	$I_{CM}$	1.5	
Collector Power Dissipation	$T_a=25^{\circ}\text{C}$	$P_C$	1	W
	$T_c \leq 60^{\circ}\text{C}$		6.5	
Junction Temperature		$T_j$	150	$^{\circ}\text{C}$
Storage Temperature Range		$T_{stg}$	-55 ~ 150	$^{\circ}\text{C}$

Unit in mm

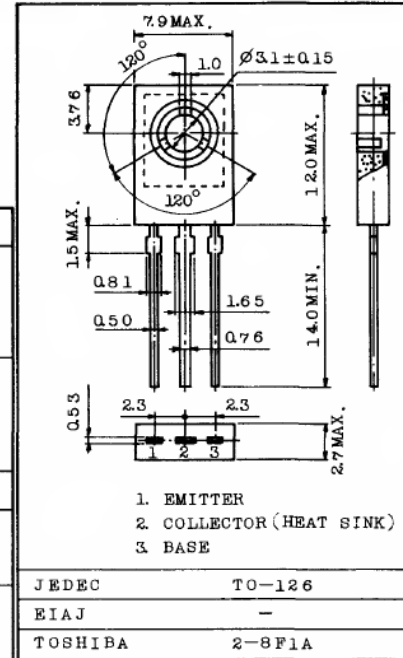

Weight : 0.72g

ELECTRICAL CHARACTERISTICS ( $T_a=25^{\circ}\text{C}$ )

CHARACTERISTIC		SYMBOL	TEST CONDITION	MIN.	TYP.	MAX.	UNIT
Collector Cut-off Current		$I_{CBO}$	$V_{CB}=30\text{V}, I_E=0$	-	-	0.1	$\mu\text{A}$
			$V_{CB}=30\text{V}, I_E=0, T_a=125^{\circ}\text{C}$	-	-	10	
Emitter Cut-off Current		$I_{EBO}$	$V_{EB}=5\text{V}, I_C=0$	-	-	10	$\mu\text{A}$
Collector-Emitter Breakdown Voltage	BD135	$V_{(BR)CEO}$	$I_C=30\text{mA}, I_B=0$	45	-	-	V
	BD137			60	-	-	
	BD139			80	-	-	
DC Current Gain		$h_{FE(1)}$	$V_{CE}=2\text{V}, I_C=5\text{mA}$	25	-	-	
		$h_{FE(2)}$	$V_{CE}=2\text{V}, I_C=150\text{mA}$	40	-	250	
		$h_{FE(3)}$	$V_{CE}=2\text{V}, I_C=500\text{mA}$	25	-	-	
Collector-Emitter Saturation Voltage		$V_{CE(sat)}$	$I_C=500\text{mA}, I_B=50\text{mA}$	-	-	0.5	V
Base-Emitter Voltage		$V_{BE}$	$V_{CE}=2\text{V}, I_C=500\text{mA}$	-	-	1.0	V
Transition Frequency		$f_T$	$V_{CE}=2\text{V}, I_C=50\text{mA}$	50	250	-	MHz

TOSHIBA CORPORATION